



ELEX 3120/3321: Electric Circuits 2

LAB 6 – Non Ideal

Student Name: Enze Xu	Student Number:A01336393	Set:B
-----------------------	--------------------------	-------

Table of Contents

1	Introduction	3
2	Experiments	3
2.1	Op-Amp Parameters	3
2.2	Slew Rate	3
2.3	Input Offset Voltage	4
2.4	Input Bias Current	4
2.5	Open and Close Loop Gain	5
3	Conclusions	8

Table of Figures

Figure 1 - Slew Rate Schematic	3
Figure 2 - Input Offset Voltage Schematic	4
Figure 3 - Input Bias Current Schematic	4
Figure 4 - Open Loop Gain Schematic	5
Figure 5 - Close Loop Gain Schematic	5
Figure 6 - Predicted and Measured Voltage Gain	6

Table of Tables

Table 1 - TL084 Parameters	3
Table 2 – LM741 Parameters	3
Table 3 - Frequency Response Table from Excel	7

1 Introduction

Operational amplifiers (op-amps) are essential components in electronic circuits, widely used for signal amplification and processing. However, their performance is influenced by non-ideal characteristics such as slew rate, input offset voltage, input bias current, and variations in open-loop and closed-loop gain. This lab explores these non-ideal properties using the LM741 and TL084 op-amps. By comparing measured parameters with datasheet specifications, this experiment aims to deepen understanding of op-amp limitations and their impact on circuit behavior.

2 Experiments

2.1 Op-Amp Parameters

	Slew Rate	Input Offset Voltage	Input Bias Current	AOL
Units	$V/\mu s$	mV	pA	V/mV
Typical	13	3	30	200
Maximum	-	6	200	-

Table 1 - TL084 Parameters

	Slew Rate	Input Offset Voltage	Input Bias Current	AOL
Units	$V/\mu s$	mV	pA	V/mV
Typical	0.5	1	80	200
Maximum	-	5	500	-
Measured	0.65	1.8	95	198

Table 2 – LM741 Parameters

2.2 Slew Rate

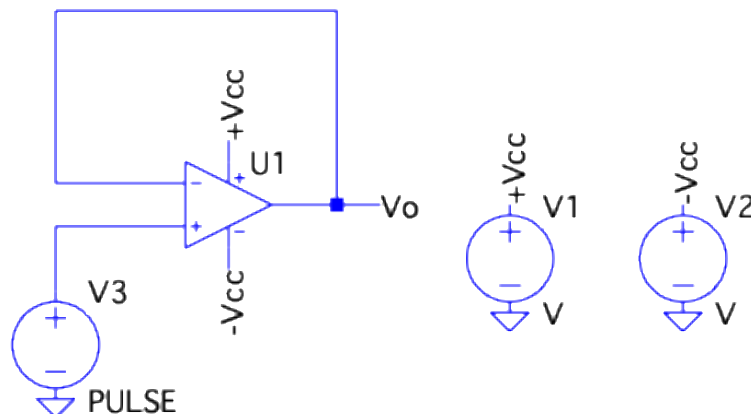


Figure 1 - Slew Rate Schematic

$$SR = \frac{\Delta V_{out}}{\Delta t}$$

2.3 Input Offset Voltage

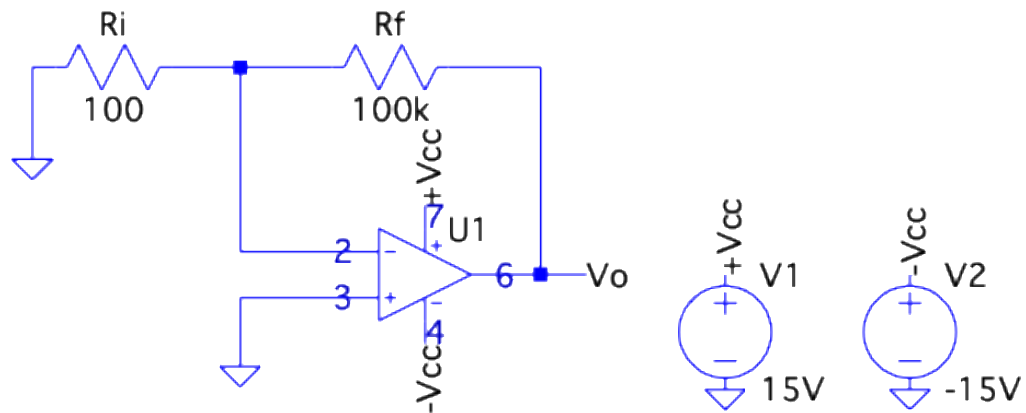


Figure 2 - Input Offset Voltage Schematic

2.4 Input Bias Current

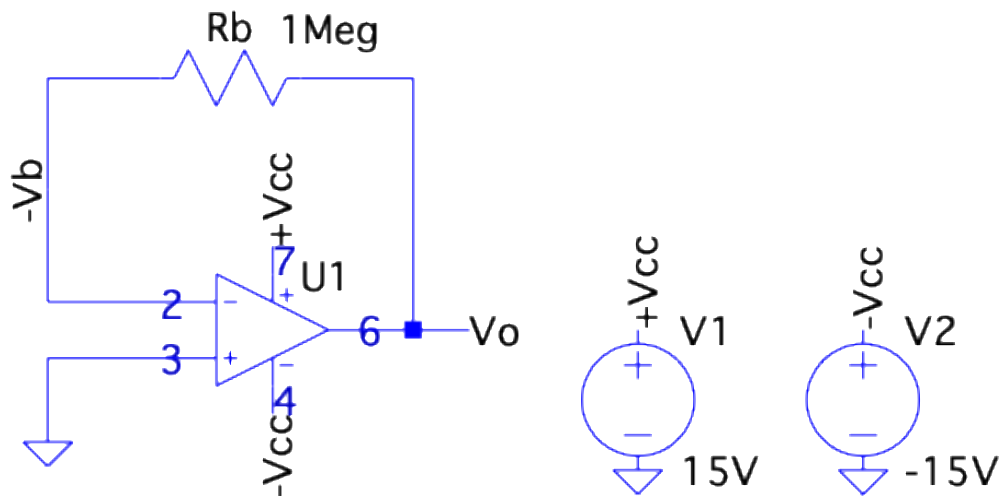


Figure 3 - Input Bias Current Schematic

2.5 Open and Close Loop Gain

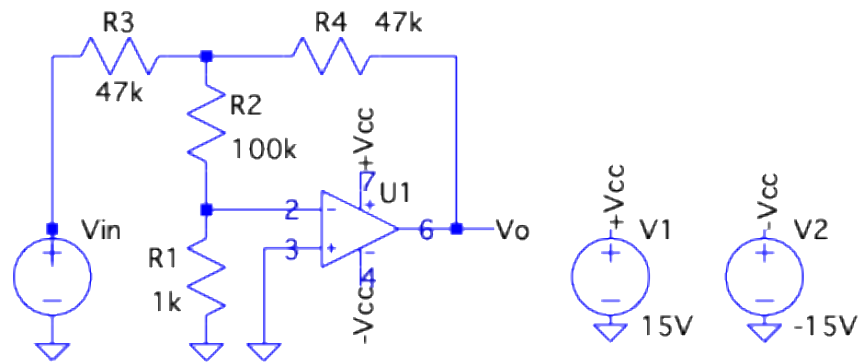


Figure 4 - Open Loop Gain Schematic

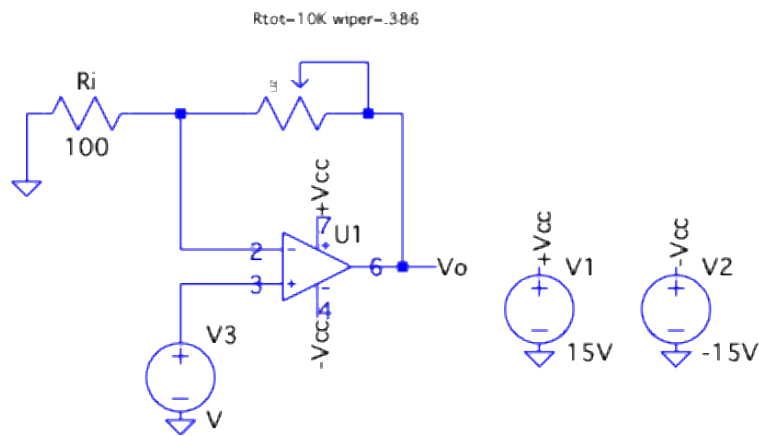


Figure 5 - Close Loop Gain Schematic

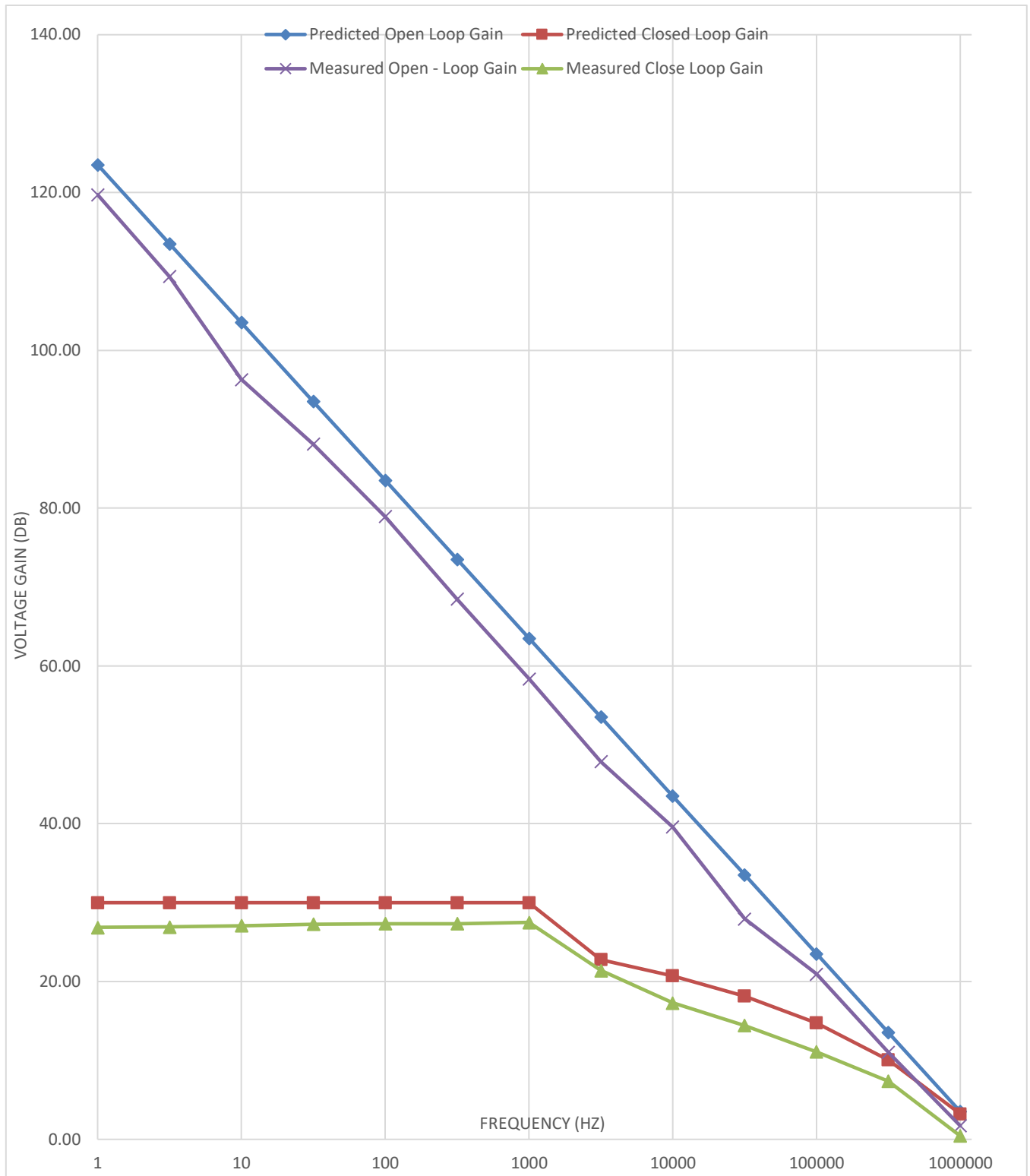


Figure 6 - Predicted and Measured Voltage Gain

Frequency (Hz)	Predicted Open-Loop Gain (AOL)	Predicted Closed-Loop Gain (ACL)	Measured Open-Loop Gain (AOL)	Measured Closed-Loop Gain (ACL)
1	123.52	30.00	119.72	26.87
3.16227766	113.52	30.00	109.36	26.91
10	103.52	30.00	96.32	27.07
31.6227766	93.52	30.00	88.12	27.27
100	83.52	30.00	78.94	27.33
316.227766	73.52	30.00	68.47	27.34
1000	63.52	30.00	58.38	27.5
3162.27766	53.52	22.77	47.88	21.39
10000	43.52	20.74	39.59	17.28
31622.7766	33.52	18.16	27.94	14.44
100000	23.52	14.76	20.96	11.1
316227.766	13.52	10.08	11.05	7.37
1000000	3.52	3.23	1.72	0.43
		UGBW		1500000
		Gnf		39.62342211

Table 3 - Frequency Response Table from Excel

3 Conclusions

This lab successfully demonstrated the measurement and analysis of non-ideal properties of op-amps. The results revealed deviations in slew rate, input offset voltage, input bias current, and gain from ideal values, emphasizing the practical limitations of real-world components. Comparing measured data with datasheet values and pre-lab predictions reinforced the importance of considering these non-idealities in circuit design.